

HW6.7 MATLAB

Consider the common emitter BJT amplifier shown below with $\beta = 100$. Assume all capacitors can be treated as short circuits at the frequency of the source V_s .

1. Draw the DC equivalent circuit and calculate the DC bias point (I_{CQ} and V_{CEQ}).
2. Draw the AC equivalent circuit and calculate the small signal voltage gain (V_O/V_S).

Note that part 1 and part 2 (a and b) are contained in my hand calculations for this assignment.

3. Create a MATLAB program to plot the DC and AC load lines on the same graph (i.e. to scale).

```
%DC load line
xint = 5;
yint = 0.68e-3;

%AC load line:
xintA = 2.98;
yintA = 1.89e-3;

hold on
plot (xint, 0, "o", 0, yint, "o" );
%This annotation should display
annotation("line", [0.1268 0.9036], [0.3823 0.1095])

plot (xintA, 0, "o", 0, yintA, "o" );
%this annotation should display the AC load line
annotation("line", [0.125 0.5929], [0.8728 0.1095])

title ("AC vs DC load lines")
xlabel("Voltage (v)")
ylabel("Ic current (A)")
```

